

# Light dependent oscillator

**Wadhwani Electronics Lab**

Department of Electrical Engineering  
Indian Institute of Technology Bombay  
2018

- \* In this experiment, we will design a light dependent frequency oscillator using CMOS inverter IC HCF4007UBE.

# Theory and Design Procedure

A practical CMOS inverter does not switch output states instantly as we change the input state. Due to presence of parasitic components  $r_{on}, r_{op}$  (drain source ON resistance) and  $c_p$  it will take a finite non-zero time to charge the output node to  $V_{DD}$  or to discharge it to zero volts.

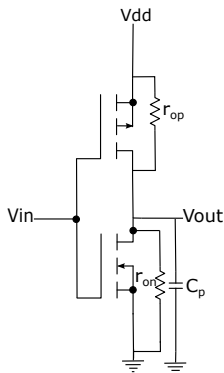


Figure: Practical CMOS inverter

# Theory and Design Procedure

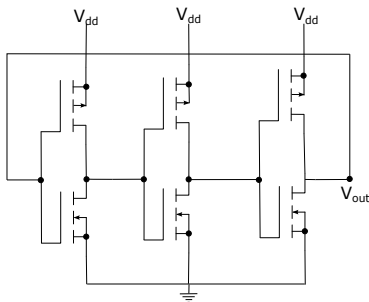


Figure: Ring Oscillator

- We use this delay of inverter to make a ring oscillator.
- Ring oscillator is formed by connecting ' $N$ ' (' $N$ ' should be odd) number of inverters back to back such that input of one inverter is connected to output of previous inverter.
- If delay of one stage is  $\tau$ , then frequency  $F$  of the oscillator is given by

$$F = \frac{1}{2 \times \text{total delay due to inverters}} = \frac{1}{2 \times N \times \tau} \quad (1)$$



Figure: Light dependent resistor


- A Light Dependent Resistor (LDR) is also called a photoresistor or a cadmium sulfide (CdS) cell. The snake like track shown below is the Cadmium Sulphide (CdS) film.
- It works on the principle of photoconductivity.
- The value of the resistance decreases as the intensity of light increases.
- Some of its applications include camera light meters, street lights, clock radios, light beam alarms, reflective smoke alarms, and outdoor clocks.

## Part A- Ring oscillator

- Make connections for an inverter.
- Set  $V_{DD}$  as 5 V and vary  $V_{in}$  from 0 to 5 V and measure  $V_{out}$ .
- Plot input-output voltage characteristics of the inverter.
- Make connections for ring oscillator as explained in theory and design procedure.
- Measure frequency of the ring oscillator and calculate delay due to one inverter.
- Make sure that now the  $V_{DD}$  is 1.5 V
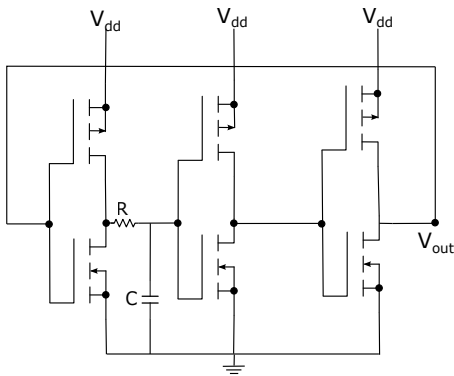
## Part B- Introducing delay in oscillator

- Use a RC series connection (as shown in the figure below) to add delay in one of the inverters in the ring oscillator.
- Use  $R = 15K\Omega$ , measure frequency of the ring oscillator for  $C = 100pF$  and  $200pF$ .
- Calculate delay for one stage of inverter by comparing time period for the two RC configurations mentioned above (use delay due to RC as  $5 \times R \times C$ ). Compare this delay with the previously calculated delay.



- Measure characteristics of LDR in different light settings.
- Replace resistor (R) in the previous circuit of ring oscillator with LDR that has been provided to you.
- Measure different frequencies of oscillator by changing intensity of light on LDR.