

Simulation Exercise: Effect of series and shunt resistance

Download the model file for solar cell from downloads Write ngSPICE netlist to plot I/V characteristics for the same for following conditions with the input voltage varied from -2V to 2V:

1. Dark
2. Lighted characteristics for the intensities corresponding to light generated current $I_L = 8 \text{ mA}$ and 10 mA .
3. Obtain the values of ideality factor , V_{oc} , I_{sc} , and fill factor in each case.

For $I_L=10 \text{ mA}$,

1. Plot I/V characteristics for series resistance $R_S = 0, 10, \text{ and } 30 \Omega$. You may plot the part of characteristic in fourth quadrant in the first quadrant for convenience.
2. What do you observe?
3. Plot I/V characteristics for shunt resistance $R_{sh} = 100\Omega, 500\Omega, \text{ and } 5K\Omega$.
4. What do you observe?
5. Explain your observations in both the cases.