

EE225 Network Theory

Tutorial Problems- Set Four

August 26, 2017













- Q1. The network shown in Fig. 1.1 and 1.2 are simple representations of a transistor. For each of these networks, determine the Thevenin equivalent seen by the load R_L .
- Q2. Determine the Thevenin equivalents and Norton equivalents of the networks shown in Fig. 2.1 and Fig. 2.2 at the terminals T shown.
- Q3. (a) The voltage source $v(t)$ in Fig. 3 is sinusoidal with angular frequency ω . Obtain the Thevenin impedance as seen at the terminal T, in terms of ω . Find the value of the load resistor R_L that ought to be connected at T (again as a function of ω) to draw the maximum power from the rest of the circuit.
(b) Now let $v(t)$ be an arbitrary voltage source with Laplace Transform $V(s)$. Use the Thevenin equivalent to obtain the Laplace transform of the current in the load resistor for a unit step input voltage.
- Q4. In the circuit of Fig. 4, obtain the value of R_3 which would draw the maximum power from the circuit when switch K is
(a) Open
(b) Closed
Now repeat parts (a) and (b) when the 100V DC source is replaced by a source of voltage $v(t) = 100 \sin(10\pi t)$
- Q5. Use Thevenin's Theorem to find the condition under which the Wheatstone bridge of Fig. 5 is balanced (i.e has no current flowing through the ammeter A).
- Q6. Find the Thevenin and Norton equivalents of the circuits shown in Figs. 6.1, 6.2, 6.3, 6.4 and 6.5 between the points a and b . Hence or otherwise obtain the current that would flow through a 10Ω resistor connected between points a and b .
- Q7. The network in Fig. 7 consists of a resistor and capacitor in addition to various controlled sources.
(a) With respect to the load consisting of a series resistor R_L and inductor L , determine the Thevenin equivalent network.
(b) Obtain the total energy, or average power, as appropriate, transferred to the load, as a function of the load parameters.
(c) Investigate whether it is possible to maximize the power transferred to the load, under three different conditions: R_L variable, L variable, both variable. (This could be tedious. There is a more **general challenging problem:** are there specific cases in which one can come up with a maximum power transfer criterion for excitations other than DC and sinusoidal ? In some specific cases, for simple circuits, one could possibly come up with solutions. You are encouraged to try and come out with some. **Rewards await good attempts).**
- Q8. Find the conditions that should exist among the constants K_1 , K_2 and the resistors R_1 , R_2 so that the network shown in Fig. 8 is reciprocal as seen from the terminal pairs ab and cd .

Q9. In Fig. 9, when a current source of 5A is connected at terminal pair B_1B_2 with current flowing from B_2 to B_1 , the voltage established at the other ports are $V_{A1A2} = -10V$, $V_{C1C2} = +15V$, $V_{D1D2} = -20V$. Current sources are now to be connected at the three pairs of terminals A, C and D while that at B is to be removed. If the currents in the three sources are 10A, 15A and 20A; how and where should they be connected in order that the power consumed in the 2Ω resistance be

- (a) Maximum
- (b) Minimum

Q10. The network shown in Fig. 10 consists of constant resistances only. When $I_1 = 5A$ and $I_2 = 10A$, $V_{ab} = 120V$. When $I_1 = 10A$ and $I_2 = 5A$, $V_{ab} = 15V$.

- (a) Find V_{ab} when $I_1 = I_2 = 10A$.
- (b) Find I_1 when $V_{ab} = 45V$, $I_2 = 5A$.
- (c) Show that a value of k exists such that if $I_1 = kI_2$, $V_{ab} = 0$ and find this value

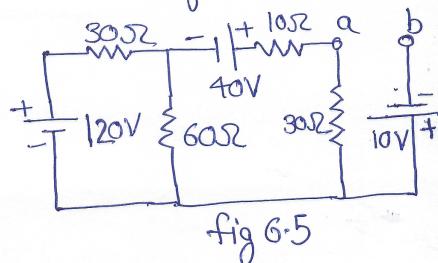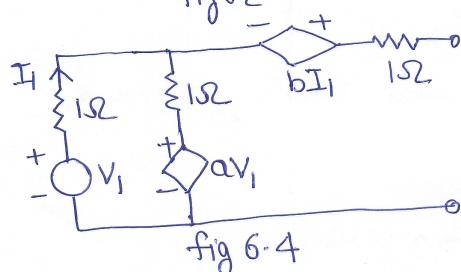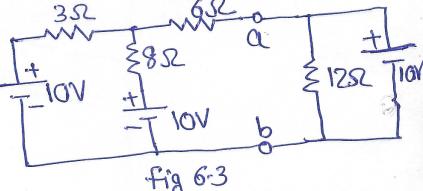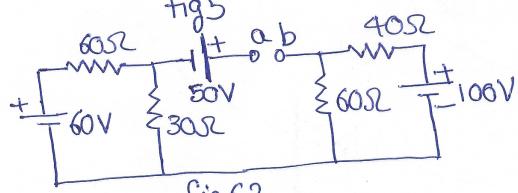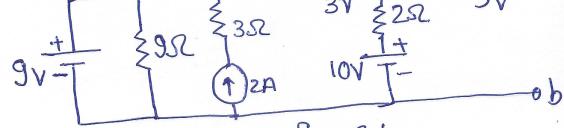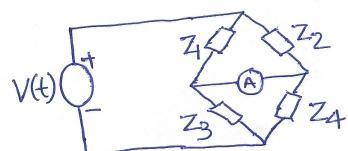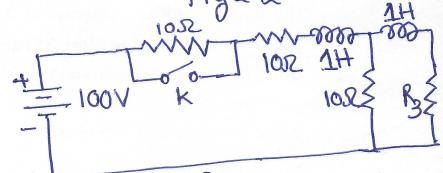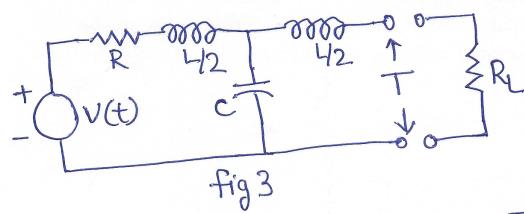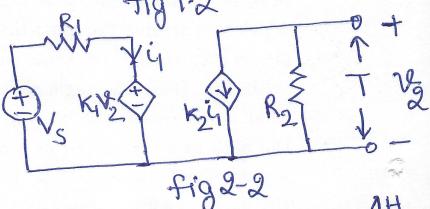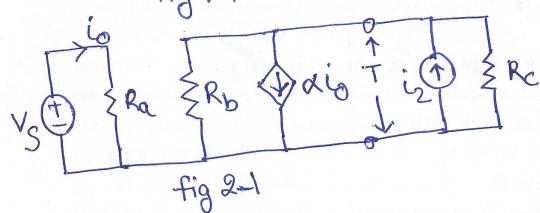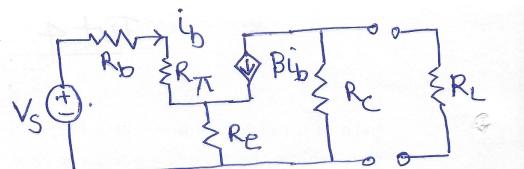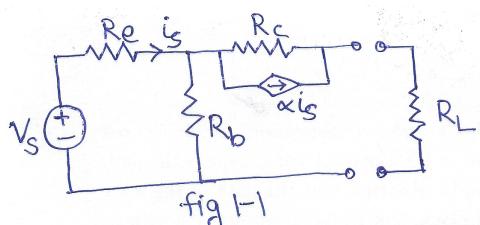

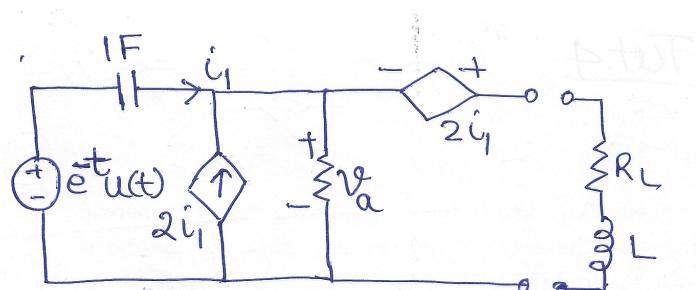


fig 7

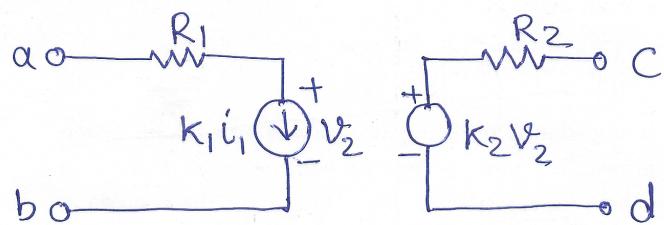


fig.8

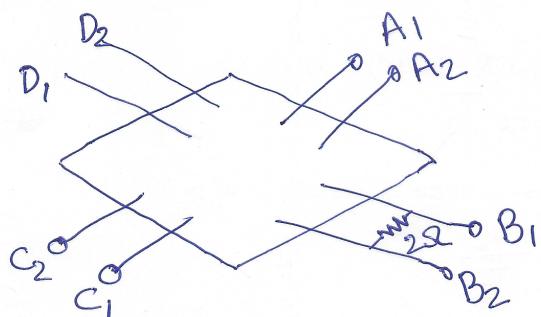


fig.9

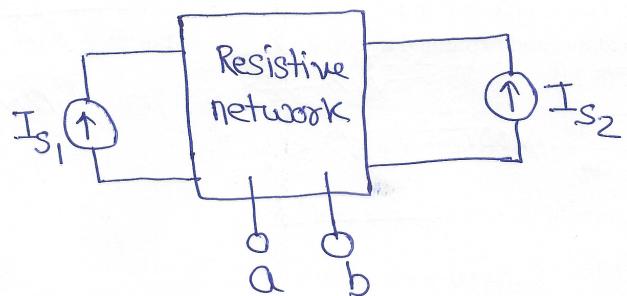


fig.10