

Simulation Exercise: RC circuits

1. Write ngspice netlist for the RC circuit shown in Fig.1. Note: $R=1\text{K}\Omega$ and $C=1\mu\text{F}$

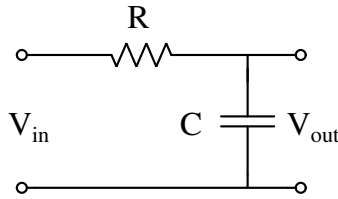


Figure 1: RC circuit 1 for simulation

2. Apply a square wave input of $10V_{PP}$ and 100Hz that varies from -5V to $+5\text{V}$.
3. Observe the input and output waveforms for 100Hz , 1Hz , 10kHz , and 100kHz .
4. Explain your observations.
5. Now add a DC offset of $+5\text{V}$ so that V_{in} varies from 0 to 10V .
6. Observe the input and output waveforms for 100Hz , 1Hz , 10kHz , and 100kHz .
7. Change the duty cycle of the input voltage to 10% and repeat step 10.
8. Modify the circuit as shown in Fig.2. and repeat the steps 1 to 7 for this circuit.
9. Explain your observations.

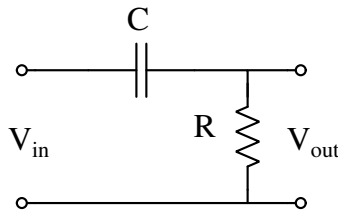


Figure 2: RC circuit 2 for simulation